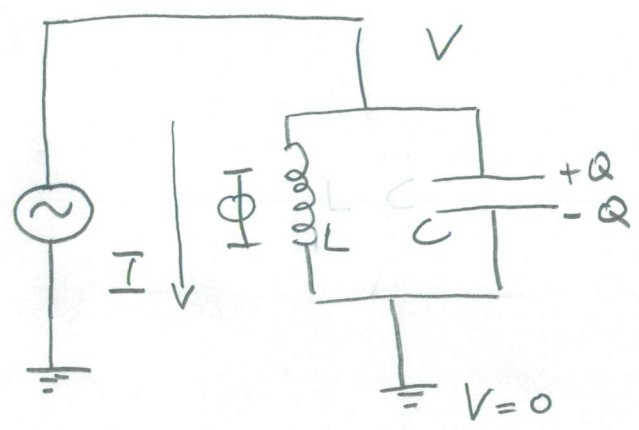


# Quantum Information Processing with Electronic Circuits

goal: learn how to construct and operate electronic circuits that behave according to the laws of quantum mechanics

- discuss:
- basic circuit elements and basic circuits
    - ↳ harmonic oscillator
    - ⇒ store photons on a chip
  - role of ⇒ discuss q.m. description of LC oscillator
  - role of dissipation
  - role of temperature

# Electronic Harmonic Oscillator



↑ V

Compare to mechanical oscillator. Which are the corresponding quantities?

- charge on capacitor

$$Q = CV$$

- flux in inductor

$$\Phi = LI$$

- Voltage across oscillator


$$V = \frac{Q}{C} = -LI = -\dot{\Phi}$$

## Hamiltonian

$$H = \frac{CV^2}{2} + \frac{LI^2}{2} = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$


electrostatic energy      magnetic energy
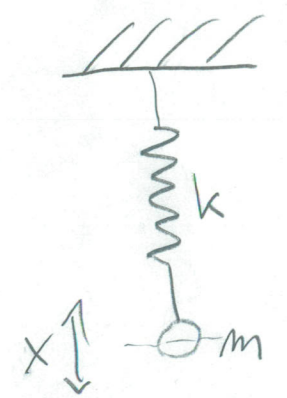
## compare to mechanical harmonic oscillator



$$H = \frac{p^2}{2m} + \frac{kx^2}{2}$$

kinetic energy      potential energy

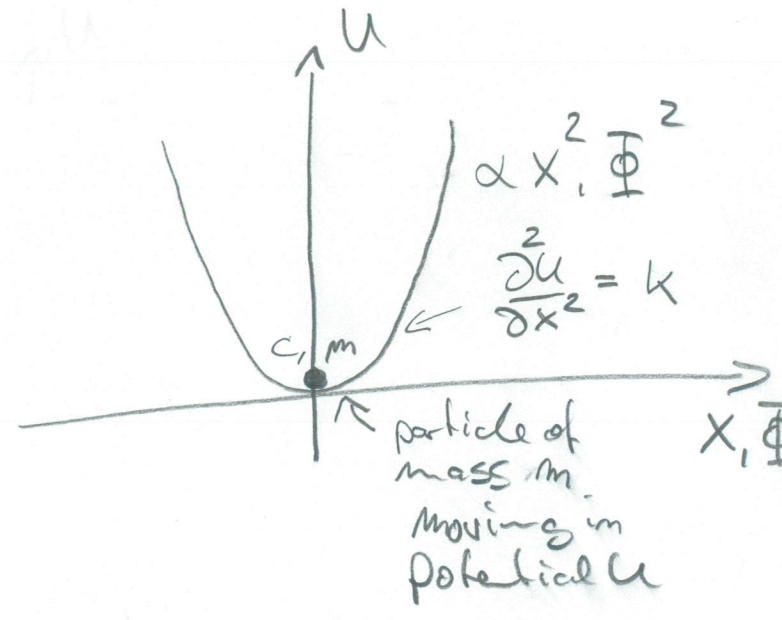

# Characteristic Quantities

## mechanical

Position  $X$

Momentum  $P$

Mass  $m$

Spring constant  $k$

resonance frequency  $\omega = \sqrt{\frac{k}{m}}$

## electronic

flux  $\Phi$   
charge  $Q$

Capacitance  $C$

inverse inductance  $\frac{1}{L}$

$\omega = \frac{1}{\sqrt{LC}}$

## harmonic oscillator

conjugate variables

$$\frac{\partial H}{\partial \Phi} = \frac{\Phi}{L} = I = \dot{Q}$$

$$\frac{\partial H}{\partial Q} = \frac{Q}{C} = V = -L\dot{I} = -\dot{\Phi}$$

• quantum mechanical operators:

$$\hat{X} = X$$

$$\hat{P} = -i\hbar \frac{\partial}{\partial X}$$

$$\hat{\Phi} = \Phi$$

$$\hat{Q} = -i\hbar \frac{\partial}{\partial \Phi}$$

We know how to quantize mechanical oscillator

• Commutation relations

$$[\hat{X}, \hat{P}] = i\hbar$$

$$[\hat{\Phi}, \hat{Q}] = i\hbar$$

flux - charge

$$\Leftrightarrow \left[ 2\pi \frac{\hat{\Phi}}{\Phi_0}, \frac{\hat{Q}}{2e} \right] = [\hat{\delta}, \hat{N}] = i$$

phase - number



# Hamilton Operator

- using conjugate variables  $Q, \Phi$

$$\hat{H} = \frac{\hat{Q}^2}{2C} + \frac{\hat{\Phi}^2}{2L} = -\frac{\hbar^2}{2C} \frac{\partial^2}{\partial \Phi^2} + \frac{1}{2L} \hat{\Phi}^2$$

- using creation and annihilation operators

$$\hat{a}^+ = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q}^+ - i \hat{\Phi}^+) \quad \text{creation operator}$$

$$\hat{a} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q} + i \hat{\Phi}) \quad \text{annihilation operator}$$

with  $Z_c = \sqrt{L/C}$  impedance of oscillator

$$\hat{H} = \hbar \omega (\hat{a}^+ \hat{a} + \frac{1}{2})$$


# Properties of $\hat{a}^\dagger$ and $\hat{a}$

$$\hat{a}^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle$$

$$\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$$

$$\hat{a}^\dagger \hat{a} |n\rangle = n |n\rangle$$

with  $|n\rangle$  number (Fock) state of harmonic oscillator

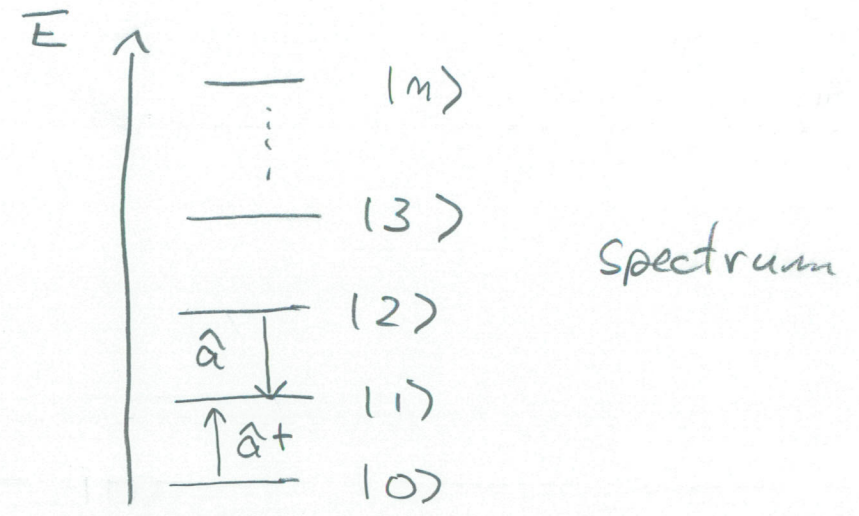

• relation to  $\hat{Q}$  and  $\hat{\Phi}$

$$\hat{Q} = \sqrt{\frac{\hbar}{2Z_c}} (\hat{a}^\dagger + \hat{a})$$

↳ relates to electric field stored on capacitor

$$\hat{\Phi} = i \sqrt{\frac{\hbar Z_c}{2}} (\hat{a}^\dagger - \hat{a})$$

↳ relates to magnetic field stored in inductor

or 
$$\hat{V} = \sqrt{\frac{\hbar \omega}{2C}} (\hat{a}^\dagger + \hat{a})$$


$$\hat{I} = i \sqrt{\frac{\hbar \omega}{2L}} (\hat{a}^\dagger - \hat{a})$$

with  $\omega = \frac{1}{\sqrt{LC}}$  and  $V = \frac{Q}{C}$  and  $I = \frac{\Phi}{L}$


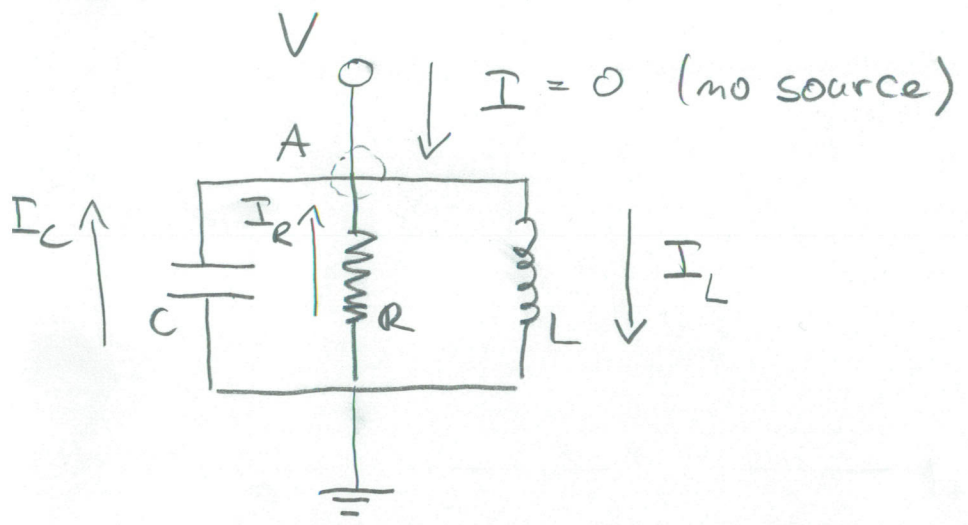
# Dissipation in the Harmonic Oscillator

What is the role of dissipation in an electrical oscillator? How does it arise?



with  
• current through resistor

$$I_R = V/R$$

• displacement current

$$I_C = \dot{Q}_C = C \dot{V}$$

• voltage across inductor

$$V = -L \dot{I}_L$$

• Kirchoff law at point A

$$I_L = I_R + I_C + I$$

$$\Leftrightarrow -C \dot{V} - \frac{V}{R} + I_L = 0 \quad (\text{same voltage at A})$$

$$\Leftrightarrow \boxed{\ddot{I}_L + \frac{1}{RC} \dot{I}_L + \frac{1}{LC} I_L = 0}$$

differential equation for current through inductor

• solutions

$$I_L(t) = I_L(0) e^{\lambda t} \quad \text{with} \quad \lambda_{1,2} = \frac{1}{2LC} \left( -\frac{L}{R} \pm \sqrt{\left(\frac{L}{R}\right)^2 - 4LC} \right)$$

# Energy Decay Rate

• underdamped oscillator

$$(4LC \gg L/R)$$

$$\lambda_{1,2} = -\frac{1}{2RC} \pm i \frac{1}{\sqrt{LC}} = -\alpha \pm i \omega$$

with  $\alpha = \frac{1}{2RC} = \frac{1}{\tau}$

amplitude decay constant

$$\tau = 2RC$$

amplitude decay time

$$\omega = 1/\sqrt{LC}$$

oscillator frequency

• energy decay rate


$$E \propto \frac{1}{2} L I_L^2 \propto e^{-\frac{1}{RC} t}$$

with  $\tau_k = \frac{1}{RC}$

energy decay rate



$$\tau_k = RC$$

energy decay time

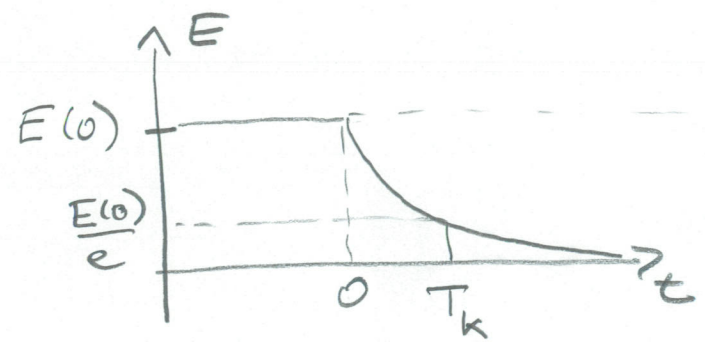

# Spectral Response of Damped Harmonic Oscillator

- driven damped oscillator

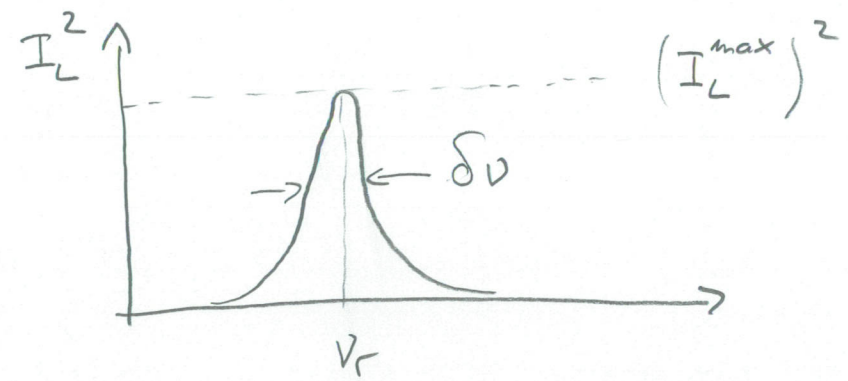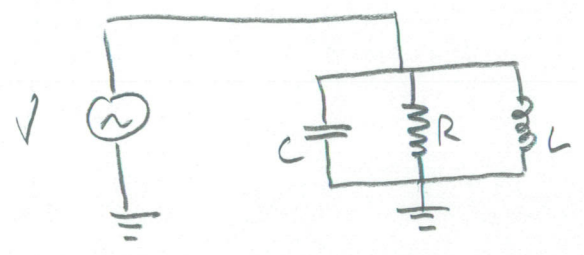


Lorentzian line shape

$$I_L^2(\nu) = (I_L^{\max})^2 \frac{\delta\nu/\pi}{(\nu - \nu_r)^2 + \delta\nu^2}$$

with  $\delta\nu$  : full width of line at half maximum



# Internal and External Dissipation

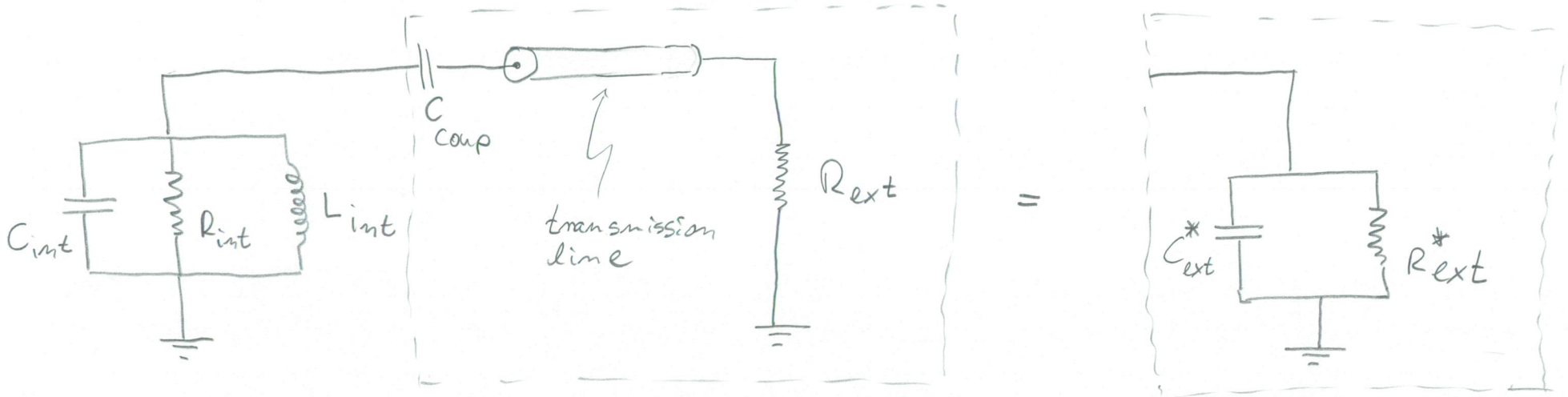

Harmonic oscillator

external circuitry

- total effective resistance  $\frac{1}{R_{tot}} = \frac{1}{R_{int}} + \frac{1}{R_{ext}^*}$   $\rightarrow$  external contribution to energy decay
- total effective capacitance  $C_{tot} = C_{int} + C_{ext}^*$   $\rightarrow$  frequency shift due to external circuit
- energy decay time of combined system  $T_k = R_{tot} C_{tot}$

Show slides on Superconductivity and realizations of harmonic oscillators

# The Josephson Junction as a Non-Linear Inductor

(1)

induction law  $V = -L \dot{I}$

Josephson equations  $I = I_0 \sin \delta$  [dc] Josephson current

$$V = \frac{\Phi_0}{2\pi} \dot{\delta} \quad \text{[ac]}$$

with

$$\dot{I} = I_0 \cos \delta \dot{\delta}$$

follows

$$V = \frac{\Phi_0}{2\pi I_0} \frac{1}{\cos \delta} \dot{I} = L_J \dot{I}$$

Josephson inductance  $L_J = L_{J0} \left( \frac{1}{\cos \delta} \right) \rightarrow$  non-linearity

$$L_{J0} = \frac{\Phi_0}{2\pi I_0} \quad \text{specific Josephson inductance}$$

Note: Phase difference  $\delta$  in Josephson junction can be regarded as normalized magnetic flux

$$\delta = 2\pi \frac{\Phi}{\Phi_0}$$

# Josephson Inductance and Josephson Energy

(2)

• Josephson energy

$$\begin{aligned} E_J &= \int V I dt \\ &= \int \frac{\Phi_0}{2\pi} \dot{\delta} I_0 \sin \delta dt \\ &= \frac{\Phi_0 I_0}{2\pi} \cos \delta \\ &= E_{J0} \cos \delta \quad \text{with } E_{J0} = \frac{\Phi_0 I_0}{2\pi} \end{aligned}$$


• typical parameters:  $I_0 = 100 \text{ nA}$

$$\Rightarrow L_{J0} = \frac{\Phi_0}{2\pi I_0} \approx 3 \text{ nH} \quad (\sim 3 \text{ mm of wire})$$

$$\Rightarrow E_{J0} = \frac{\Phi_0 I_0}{2\pi} \approx 50 \text{ GHz}$$



# The Cooper Pair Box Qubit

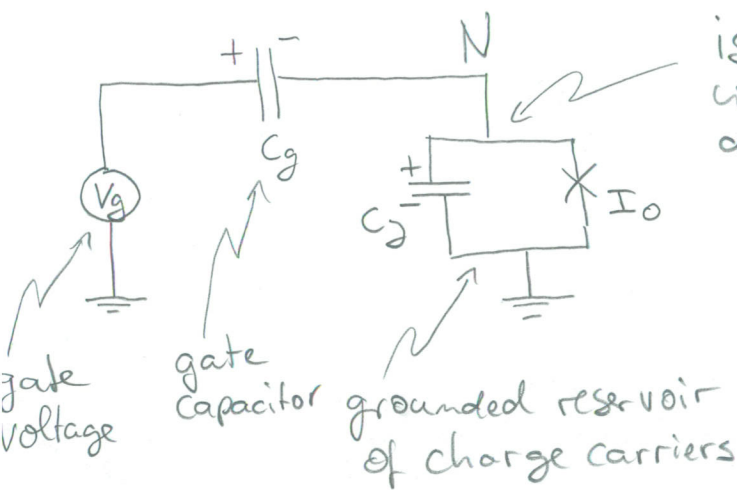

island on which charges are localized

$$N = \frac{Q}{2e}$$

discrete variable

number of Cooper pairs on island (with respect to charge neutrality)

$$N_g = \frac{C_g V_g}{2e}$$

polarization charge on gate capacitor

continuous variable


• Hamiltonian

$$H = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$

electrostatic + magnetic energy

• electrostatic energy
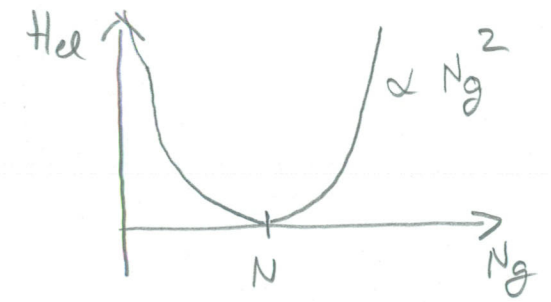
$$H_{el} = \frac{Q^2}{2C} = \frac{(2e)^2 (N - N_g)^2}{2C_{\Sigma}}$$



with  $C_{\Sigma} = C_j + C_g + \dots$  (stray capacitances)

total capacitance of island

and  $E_C = \frac{(2e)^2}{2C_{\Sigma}}$  charging energy

How does the electrostatic energy depend on the gate voltage?

• magnetic energy

$$\begin{aligned}
 H_{\text{mag}} &= -E_J \cos \delta = - \frac{\Phi_0 I_0}{2\pi} \overbrace{\cos \delta}^{\approx 1 - \frac{\delta^2}{2} + \dots} \\
 &\approx - \frac{\Phi_0 I_0}{2\pi} \left( 1 - \frac{1}{2} \left( \frac{\Phi}{\Phi_0} 2\pi \right)^2 + \dots \right) \\
 &\approx \frac{1}{2} \frac{\Phi^2}{L J_0} \quad (\text{standard expression for mag. energy})
 \end{aligned}$$

• Cooper pair box Hamiltonian operator

$$\hat{H} = E_C (\hat{N} - N_g)^2 - E_J \cos \hat{\delta}$$

$\frac{1}{2}(e^{i\hat{\delta}} + e^{-i\hat{\delta}})$

with commutation relation  $[\hat{\delta}, \hat{N}] = i$  for conjugate variables  $\delta$  and  $N$ .

Transformation between bases:

$$|\delta\rangle = \frac{1}{\sqrt{2\pi}} \sum_N e^{iN\delta} |N\rangle$$

number states

• properties of phase  $\hat{\delta}$  and number  $\hat{N}$  operators

$$[\hat{\delta}, \hat{N}] = i \Rightarrow e^{\pm i\hat{\delta}} |N\rangle = |N \pm 1\rangle$$

number operator

$$\hat{N} |N\rangle = N |N\rangle$$

$$\sum_N |N\rangle\langle N| = \mathbb{1} \quad ; \quad \text{completeness}$$

$$\langle M | N \rangle = \delta_{M,N} \quad ; \quad \text{orthogonality}$$

# Hamilton Operator of Cooper Pair Box in Charge Basis

$$\hat{H} = \sum_N \left( \underbrace{E_C (N - N_g)^2}_{\text{energy of charges on island}} |N\rangle\langle N| - E_J/2 \left( |N\rangle\langle N+1| + |N+1\rangle\langle N| \right) \right)$$

- solve time independent Schrödinger equation in discrete charge basis  $|N\rangle$  to find energy eigenstates  $|\psi\rangle$  of qubit

Show band diag. slides!

$$\hat{H} |\psi_m\rangle = E_m |\psi_m\rangle$$

- equivalent Hamilton operator in phase basis  $\delta$  (continuous & periodic)

$$\hat{N} = \frac{\hat{Q}}{2e} = -i\hbar \frac{1}{2e} \frac{\partial}{\partial \Phi} = -i \frac{\partial}{\partial \delta}$$

$$\hat{H} = E_C \left( -i \frac{\partial}{\partial \delta} - N_g \right)^2 - E_J \cos \delta$$

$\Rightarrow$  exact solutions for  $\hat{H} \psi_m(\delta) = E_m \psi_m(\delta)$  are Mathieu functions