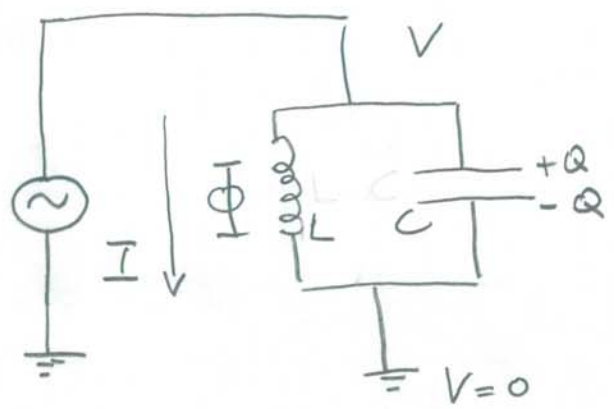


Quantum Information Processing with Electronic Circuits

goal: learn how to construct and operate electronic circuits that behave according to the laws of quantum mechanics

- discuss:
- basic circuit elements and basic circuits
 - ↳ harmonic oscillator
 - ⇒ store photons on a chip
 - role of ⇒ discuss q.m. description of LC oscillator
 - role of dissipation
 - role of temperature

Electronic Harmonic Oscillator



Compare to mechanical oscillator. Which are the corresponding quantities?

- charge on capacitor

$$Q = CV$$

- flux in inductor

$$\Phi = LI$$

- voltage across oscillator


$$V = \frac{Q}{C} = -LI = -\dot{\Phi}$$

Hamiltonian

$$H = \frac{CV^2}{2} + \frac{LI^2}{2} = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$


electrostatic energy
magnetic energy

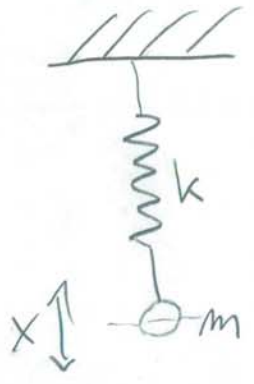compare to mechanical harmonic oscillator



$$H = \frac{p^2}{2m} + \frac{kx^2}{2}$$

kinetic energy
potential energy

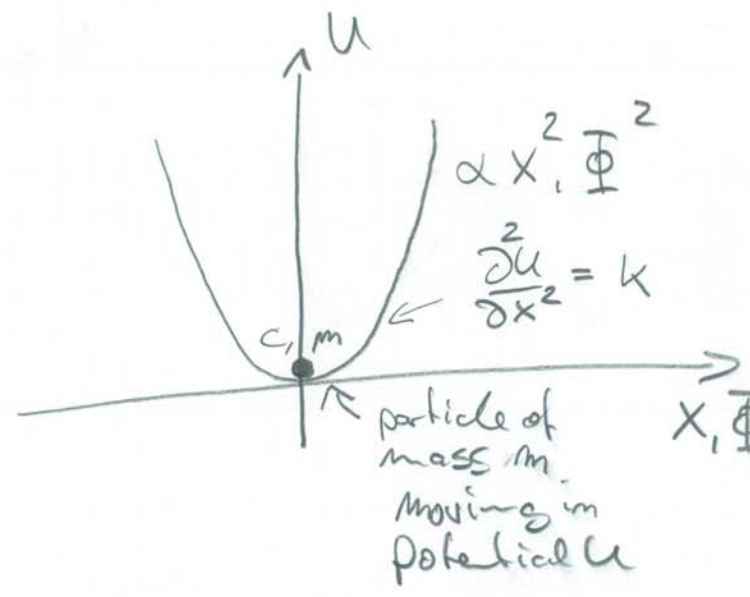

Characteristic Quantities

(2)

mechanical

Position x

Momentum p

Mass m

Spring constant k

resonance frequency $\omega = \sqrt{\frac{k}{m}}$

electronic

flux Φ

charge Q

Capacitance C

inverse inductance $\frac{1}{L}$

$\omega = \frac{1}{\sqrt{LC}}$

harmonic oscillator

conjugate variables

$$\frac{\partial H}{\partial \Phi} = \frac{\Phi}{L} = I = \dot{Q}$$

$$\frac{\partial H}{\partial Q} = \frac{Q}{C} = V = -L\dot{I} = -\dot{\Phi}$$

• quantum mechanical operators:

$$\hat{X} = x$$

$$\hat{P} = -i\hbar \frac{\partial}{\partial x}$$

$$\hat{\Phi} = \Phi$$

$$\hat{Q} = -i\hbar \frac{\partial}{\partial \Phi}$$

We know how to quantize mechanical oscillator

• commutation relations

$$[\hat{x}, \hat{p}] = i\hbar$$

$$[\hat{\Phi}, \hat{Q}] = i\hbar$$

flux - charge

$$\Leftrightarrow \left[2\pi \frac{\hat{\Phi}}{\Phi_0}, \frac{\hat{Q}}{2e} \right] = [\hat{\delta}, \hat{N}] = i$$

phase - number

Hamilton Operator

- using conjugate variables Q, Φ

$$\hat{H} = \frac{\hat{Q}^2}{2C} + \frac{\hat{\Phi}^2}{2L} = -\frac{\hbar^2}{2C} \frac{\partial^2}{\partial \Phi^2} + \frac{1}{2L} \hat{\Phi}^2$$

- using creation and annihilation operators

$$\hat{a}^{\dagger} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q}^{\dagger} - i \hat{\Phi}^{\dagger}) \quad \text{creation operator}$$

$$\hat{a} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q} + i \hat{\Phi}) \quad \text{annihilation operator}$$

$$\text{with } Z_c = \sqrt{L/C} \quad \text{impedance of oscillator}$$

$$\hat{H} = \hbar \omega \left(\hat{a}^{\dagger} \hat{a} + \frac{1}{2} \right)$$


Properties of \hat{a}^\dagger and \hat{a}

$$\hat{a}^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle$$

$$\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$$

$$\hat{a}^\dagger \hat{a} |n\rangle = n |n\rangle$$

with $|n\rangle$ number (Fock) state of harmonic oscillator

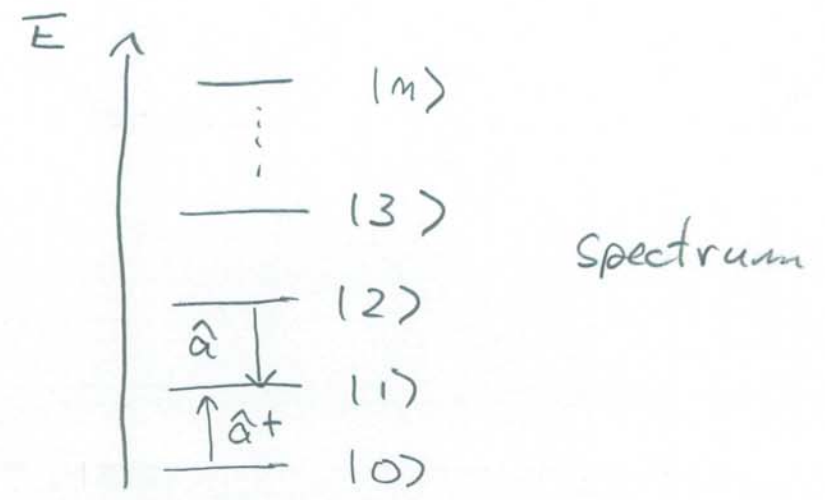

• relation to \hat{Q} and $\hat{\Phi}$

$$\hat{Q} = \sqrt{\frac{\hbar}{2Z_c}} (\hat{a}^\dagger + \hat{a})$$

\rightarrow relates to electric field stored on capacitor

$$\hat{\Phi} = i \sqrt{\frac{\hbar Z_c}{2}} (\hat{a}^\dagger - \hat{a})$$

\rightarrow relates to magnetic field stored in inductor


or
$$\hat{V} = \sqrt{\frac{\hbar \omega}{2C}} (\hat{a}^\dagger + \hat{a})$$

$$\hat{I} = i \sqrt{\frac{\hbar \omega}{2L}} (\hat{a}^\dagger - \hat{a})$$

with $\omega = \frac{1}{\sqrt{LC}}$ and $V = \frac{Q}{C}$ and $I = \frac{\Phi}{L}$

Dissipation in the Harmonic Oscillator

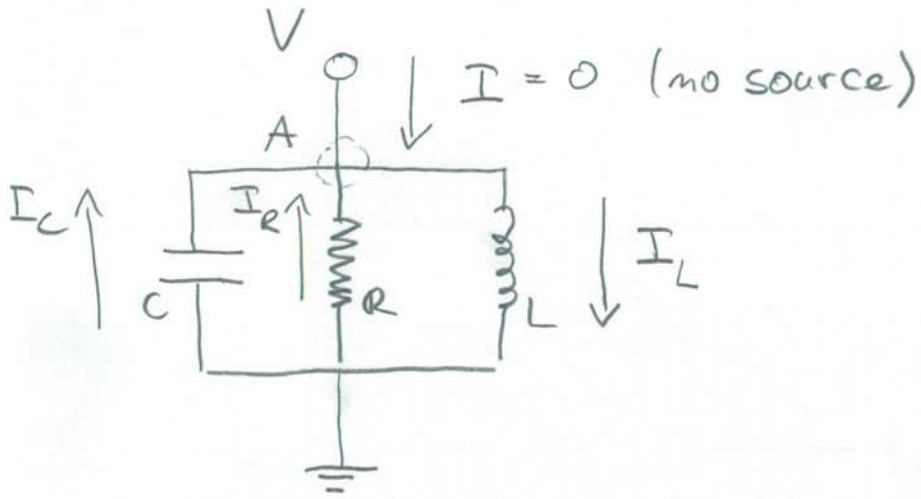What is the role of dissipation in an electrical oscillator? How does it arise?



with

- current through resistor

$$I_R = V/R$$

- displacement current

$$I_C = \dot{Q}_C = C \dot{V}$$

- voltage across inductor

$$V = -L \dot{I}_L$$

- Kirchoff law at point A

$$I_L = I_R + I_C + I$$

$$\Leftrightarrow -C \dot{V} - \frac{V}{R} + I_L = 0 \quad (\text{same voltage at A})$$

$$\Leftrightarrow \boxed{\ddot{I}_L + \frac{1}{RC} \dot{I}_L + \frac{1}{LC} I_L = 0}$$

differential equation for current through inductor

- solutions

$$I_L(t) = I_L(0) e^{\lambda t} \quad \text{with} \quad \lambda_{1,2} = \frac{1}{2LC} \left(-\frac{L}{R} \pm \sqrt{\left(\frac{L}{R}\right)^2 - 4LC} \right)$$

Energy Decay Rate

• underdamped oscillator

$$(4LC \gg L/R)$$

$$\lambda_{1,2} = -\frac{1}{2RC} \pm i \frac{1}{\sqrt{LC}} = -\alpha \pm i \omega$$

with $\alpha = \frac{1}{2RC} = \frac{1}{\tau}$

amplitude decay constant

$$\tau = 2RC$$

amplitude decay time

$$\omega = 1/\sqrt{LC}$$

oscillator frequency

• energy decay rate


$$E \propto \frac{1}{2} L I_L^2 \propto e^{-\frac{1}{RC} t}$$

with $k = \frac{1}{RC}$

energy decay rate



$$T_k = RC$$

energy decay time

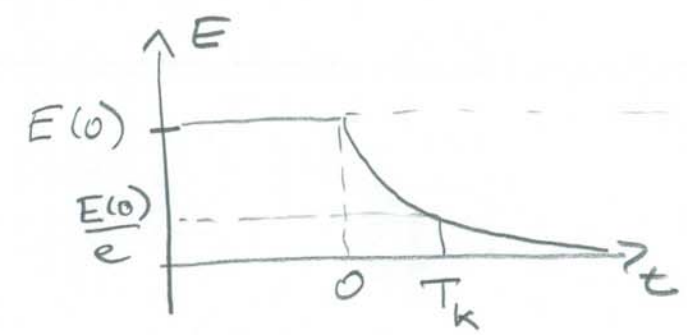

Spectral Response of Damped Harmonic Oscillator

- driven damped oscillator

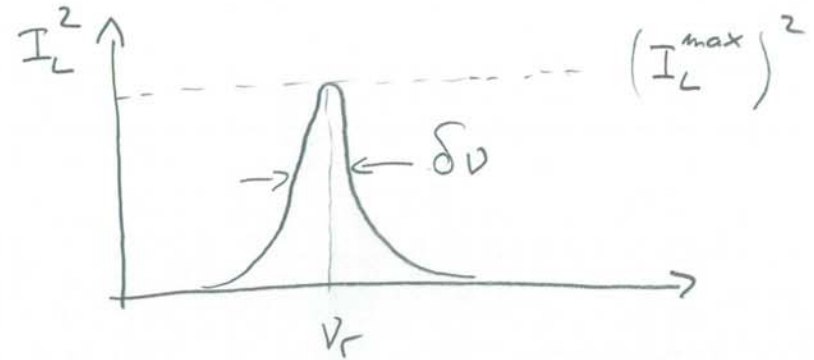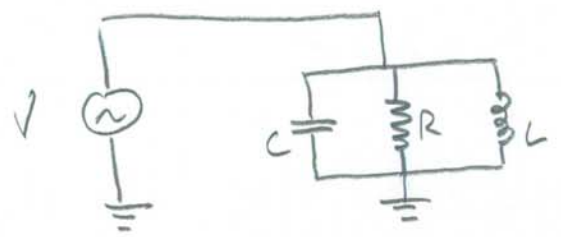


Lorentzian line shape

$$I_L^2(\nu) = (I_L^{max})^2 \frac{\delta\nu/\pi}{(\nu - \nu_r)^2 + \delta\nu^2}$$

with $\delta\nu$: full width of line at half maximum


Internal and External Dissipation

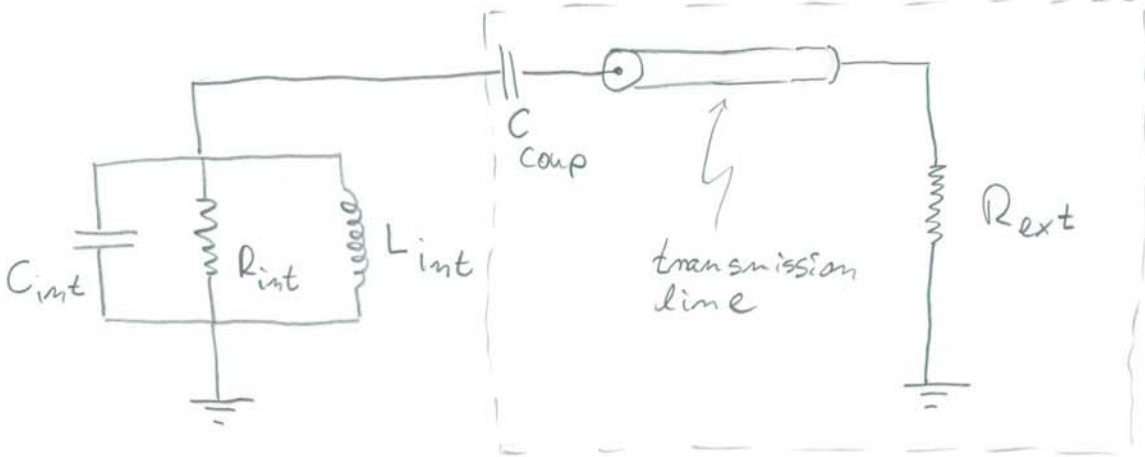

harmonic oscillator

external circuitry

=

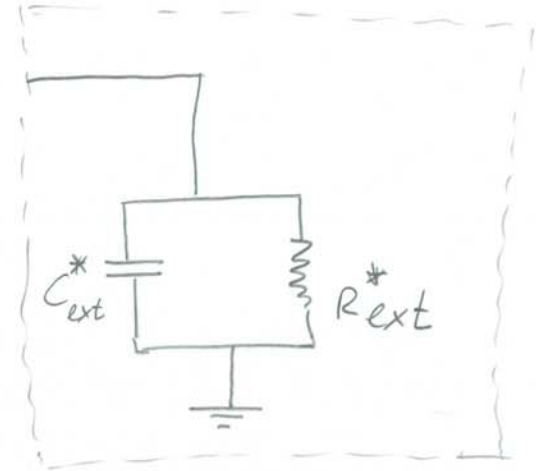

- total effective resistance $\frac{1}{R_{tot}} = \frac{1}{R_{int}} + \frac{1}{R_{ext}^*}$ \rightarrow external contribution to energy decay
- total effective capacitance $C_{tot} = C_{int} + C_{ext}^*$ \rightarrow frequency shift due to external circuit
- energy decay time of combined system $T_k = R_{tot} C_{tot}$

Show slides on Superconductivity and realizations of harmonic oscillators

The Josephson Junction as a Non-Linear Inductor

①

induction law

$$V = -L \dot{I}$$

Josephson equations

$$I = I_0 \sin \delta \quad \boxed{\text{dc}}$$

$$V = \frac{\Phi_0}{2\pi} \dot{\delta} \quad \boxed{\text{ac}}$$

with

$$\dot{I} = I_0 \cos \delta \dot{\delta}$$

follows

$$V = \frac{\Phi_0}{2\pi I_0} \frac{1}{\cos \delta} \dot{I} = L_J \dot{I}$$

Josephson inductance

$$L_J = L_{J0} \left(\frac{1}{\cos \delta} \right) \rightarrow \text{non-linearity}$$

$$L_{J0} = \frac{\Phi_0}{2\pi I_0}$$

specific Josephson inductance

Note: Phase difference δ in Josephson junction can be regarded as normalized magnetic flux

$$\delta = 2\pi \frac{\Phi}{\Phi_0}$$

Josephson Inductance and Josephson Energy

(2)

• Josephson energy

$$\begin{aligned} E_J &= \int V I dt \\ &= \int \frac{\Phi_0}{2\pi} \dot{\delta} I_0 \sin \delta dt \\ &= \frac{\Phi_0 I_0}{2\pi} \cos \delta \\ &= E_{J0} \cos \delta \quad \text{with } E_{J0} = \frac{\Phi_0 I_0}{2\pi} \end{aligned}$$

• typical parameters: $I_0 = 100 \text{ mA}$

$$\Rightarrow L_{J0} = \frac{\Phi_0}{2\pi I_0} \approx 3 \text{ mH} \quad (\sim 3 \text{ mm of wire})$$

$$\Rightarrow E_{J0} = \frac{\Phi_0 I_0}{2\pi} \approx 50 \text{ GHz}$$